

DON'T CARE CONDITIONS

- Functions that have unspecified output for some input combinations are called incompletely specified functions.
- Unspecified minterms of a functions are called ‘don’t care’ conditions. We simply *don’t care* whether the value of 0 or 1 is assigned to F for a particular minterm.
- Don’t care conditions are represented by X in the K-Map table.

➤ *Don’t care* conditions play a central role in the specification and optimization of logic circuits as they represent the degrees of freedom of transforming a network into a functionally equivalent one.

DON'T CARE CONDITIONS

Example: Simplify the Boolean function

$$F(w, x, y, z) = \Sigma(1,3,7,11,15), \quad dc(w, x, y, z) = \Sigma(0,2,5)$$


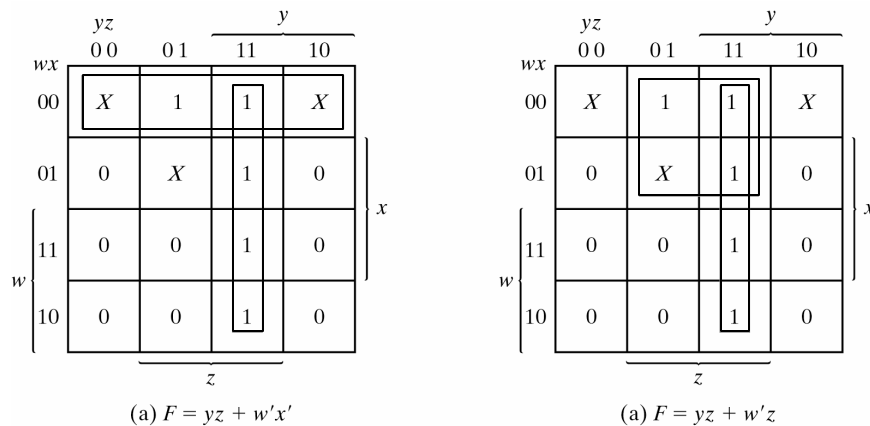


Fig. 3-17 Example with don't-care Conditions


Implementing Logic Circuits with NAND

 Example: $F(x, y, z) = \Sigma(1,2,3,4,5,7)$




Implementing Logic Circuits with NAND

Multi-Level Gate Implementation

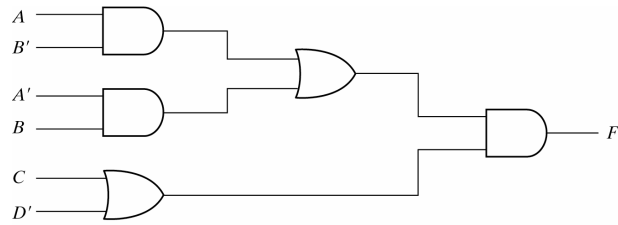


(a) AND-OR gates

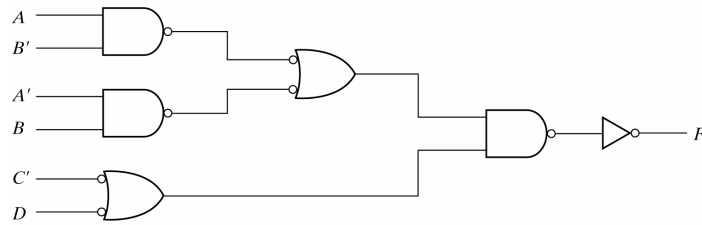


(b) NAND gates

Fig. 3-23 Implementing $F = (AB' + A'B)(C + D')$


AND-OR-INVERT Gate Implementation

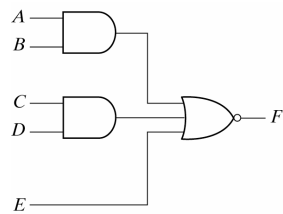

(a) AND-NOR

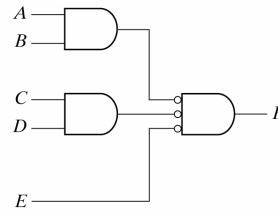

(b) AND-NOR

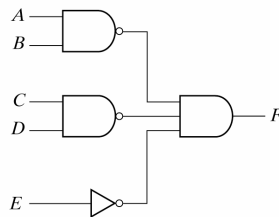

(c) NAND-AND

Fig. 3-29 AND-OR-INVERT Circuits; $F = (AB + CD + E)'$

OR-AND-INVERT Gate Implementation


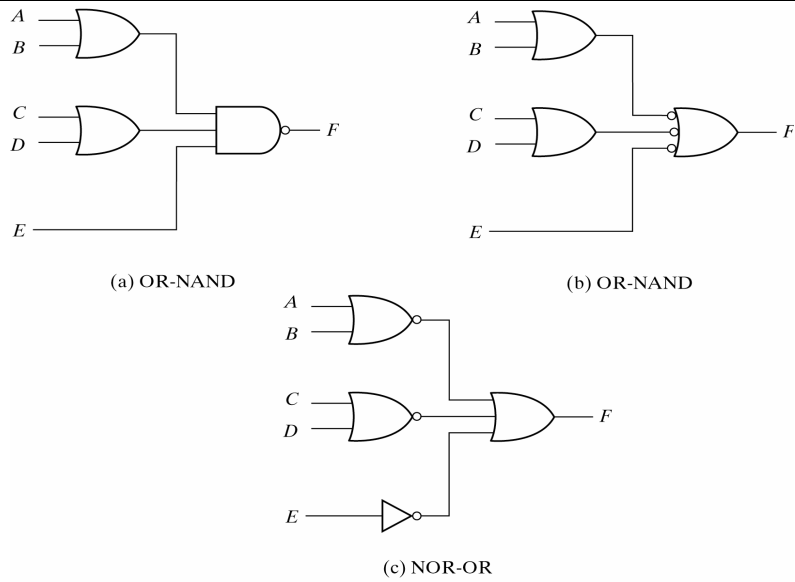
 


Fig. 3-30 OR-AND-INVERT Circuits; $F = [(A + B)(C + D)E]'$

EXCLUSIVE-OR FUNCTION

$$x \oplus y = xy' + x'y$$

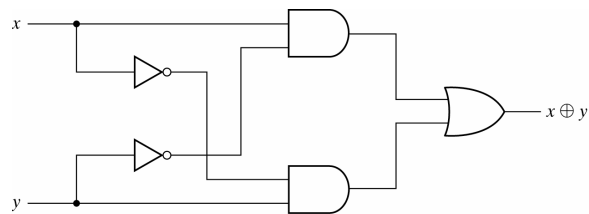

Verilog Hardware Descriptive Language

- Verilog is language that describes the hardware of digital systems in textual form.
- It can be used to represent logic diagrams, Boolean expressions, and other more complex digital circuits.
- There are two applications of HDL processing: simulation and synthesis.

1. *Logic simulation*: representation of the structure and behavior of a digital system. A simulator interprets the HDL code and produces an output that predicts the behavior of the hardware before it's actually fabricated.

2. *Logic synthesis*: process of deriving a list of components and their interconnections from the system model described in HDL. This process produces a database with instructions on how to fabricate a piece of hardware.

SynaptiCAD

C:\SynaptiCad\Examples_Book\Book_Tutorials

Or you can go directly to the VeriLogger Tutorial:
Basic Verilog Simulation

//HDL Example 3-1

//Description of the simple circuit of Fig. 3-37

```
module smpl_circuit(A,B,C,x,y);  
  input A,B,C;             
  output x,y;             
  wire e;                 
  and g1(e,A,B);          
  not g2(y,C);            
  or g3(x,e,y);           
endmodule
```

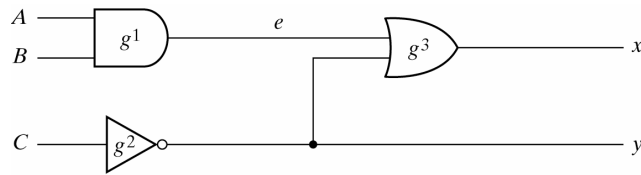


Fig. 3-37 Circuit to Demonstrate HDL

Circuit with delay in HDL

//HDL Example 3-2

//-----

//Description of circuit with delay

```
module circuit_with_delay (A,B,C,x,y);  
  input A,B,C;             
  output x,y;             
  wire e;                 
  and #(30) g1(e,A,B);    
  or #(20) g3(x,e,y);     
  not #(10) g2(y,C);      
endmodule
```

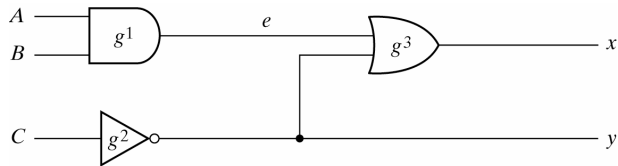


Fig. 3-37 Circuit to Demonstrate HDL

Stimulus to a design: *test bench*

```
//HDL Example 3-3
//-----
//Stimulus for simple circuit
module stimcrct;
reg A,B,C;
wire x,y;
circuit_with_delay cwd(A,B,C,x,y);
initial
  begin
    A = 1'b0; B = 1'b0; C = 1'b0;
    #100
    A = 1'b1; B = 1'b1; C = 1'b1;
    #100 $finish;
  end
endmodule
```

Simulation Output

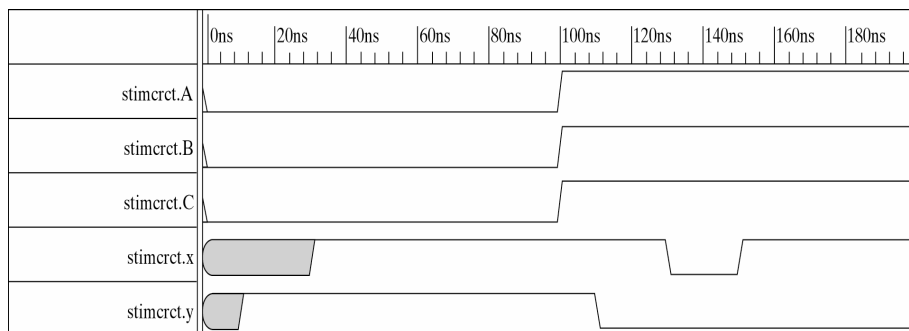


Fig. 3-38 Simulation Output of HDL Example 3-3

Boolean Algebra in Verilog HDL

$$x = A + BC + B' D$$

$$y = B' C + BC' D'$$

```
//HDL Example
//-----
//Circuit specified with Boolean equations
module circuit_bln (x,y,A,B,C,D);
  input A,B,C,D;
  output x,y;
  assign x = A | (B & C) | (~B & D);
  assign y = (~B & C) | (B & ~C & ~D);
endmodule
```